7. The "1-dimensional" wave equation and The d'Alembert Solution +*+*+*+*+*+*

Consider the equations that govern the relationship between voltage and current along a transmission line.

v(t,t) v(t,

A very useful approximation that can often be employed is to assume that R=0, and G=0.

Then the equations reduce to

$$-\frac{\partial v}{\partial z} = L\frac{\partial i}{\partial t}$$

$$-\frac{\partial i}{\partial z} = C\frac{\partial v}{\partial t}$$

$$\rightarrow \begin{cases} \frac{\partial^2 v}{\partial z^2} - LC\frac{\partial^2 v}{\partial t^2} = 0 \\ \frac{\partial^2 i}{\partial z^2} - LC\frac{\partial^2 v}{\partial t^2} = 0 \end{cases}$$

The last equation is the one dimensional wave equation and can be solved in a very elegant manner.

Suppose we set v(t, z) = f(at + bz). Then

$$\frac{\partial f}{\partial t} = af'(at+bz); \quad \frac{\partial f}{\partial z} = bf'(at+bz) \quad \text{where} \\ \frac{\partial^2 f}{\partial t^2} = a^2 f''(at+bz); \quad \frac{\partial^2 f}{\partial z^2} = b^2 f''(at+bz) \quad \int f'(z) = \frac{d^2 f(z)}{dz^2} dz$$

Substituting this into the wave equation, we find that

$$b^{2} f''(at+bz) - LC a^{2} f''(at+bz) = C$$

$$b^{2} - LC a^{2} = 0 \implies b = \pm \sqrt{LC a}$$

We can choose a=1 and the solutions to the wave equation are

$$v(t, =) = f(t + \frac{\pi}{2})$$
 and $v(t, =) = f(t - \frac{\pi}{2})$
where $c = 1/\sqrt{LC}$. The units of c are

Since the differential operators are linear, the general solution to the 1-D wave equation is $v(t,z) = f_1(t-z/c) + f_2(t+z/c).$

To solve a physical problem, we must introduce boundary conditions to obtain a unique solution.

a) Radiation condition - infinite transmission line


Physically what does the solution v(t,z) = f(t-z/c) represent?

This represents a wave that is traveling along the transmission line in the positive z direction.

It is an undistorted wave because the response at a distance z is the same as that at distance O except that it is DELAYED by z/c where c is the wave speed.

Similarly, a solution of the form v(t,z) = f(t+z/c) is a wave traveling in the negative z direction.

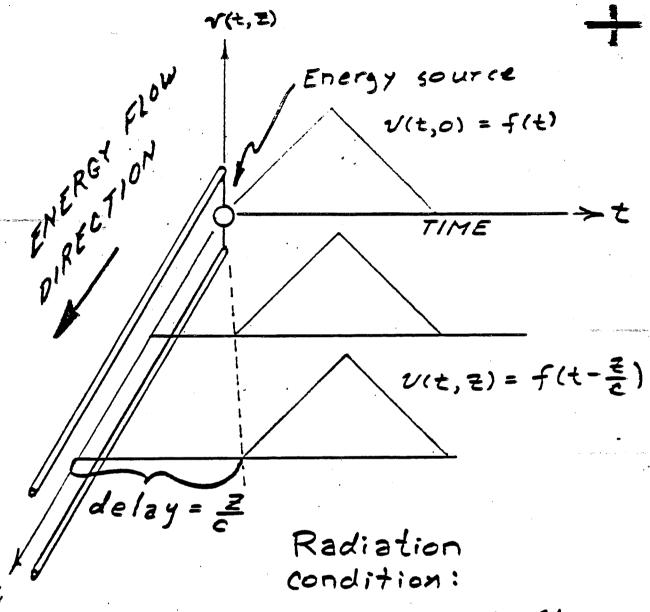Consider the uniform transmission with a source of v(t,0) = f(t) shown in figure 1.



The boundary conditions are v(t,0) = f(t). Radiation condition

Energy must flow away from the source

is excluded by the radiation condition.

+ FIG 1

b) Loaded transmission lines

To consider a loaded line, we must find how v and i are related.

Consider first a wave propagating in the $\pm z$ direction. We have seen that v(t,z) = f(t-z/c).

Since the current must satisfy exactly the same differential equation, i(t,z) = g(t-z/c).

Using the relation.

We conclude that

which implies that f(u) =
(cL)g(u).+ K where K is some
constant. That constant
represents a DC voltage between
the two parallel wires in the
line.

It is of little physical interest and is taken to be zero.

- The coefficient, cL, is -

and is called the characteristic impedance or wave impedance of the transmission line. Its reciprocal, Yo, is called the characteristic admittance.

Therefore

for waves propagating in the +z direction.

Similarly, for a wave propagating in the -z direction, the current and voltage are related by

$$v(t,z) = -3_0i(t,z) = -6_0i(t,z)$$

Therefore, in general,

$$v(t, z) = f_1(t-z/c) + f_2(t+z/c)$$

 $i(t, z) = Y_0f_1(t-z/c) - Y_0f_2(t+z/c).$

The boundary conditions for a transmission line excited by a voltage source at z=0 of f(t) and loaded at z=z, with a short are:

U(t,o) = f(t) $U(t, z_0) = 0$

We must assume <u>both</u> waves going in the + and - directions:

Applying the boundary conditions, we find that

$$f_2(t + z_0/c) = -f_1(t - z_0/c) \implies f_2(t) = -f_1(t - 2z_0/c),$$

and

$$f_{1}(t) = f(t) - f_{2}(t)$$

= $f(t) + f_{1}(t - 2z_{0}/c)$.

Therefore, we have that If f(t) = 0 for t < 0, then $f_1(t) = 0$ also for t < 0. Therefore, $f_1(t-2z_0/c) = 0$ for $t < 2z_0/c$.

Thus, for $t < 2z_0/c$, $f_1(t) = f(t)$.

For $2z_0/c < t < 4z_0/c$, $f_1(t) = f(t) + f_1(t-2z_0/c)$ $= f(t) + f(t-2z_0/c)$.


This process can be carried out infinitely many times with the result that

 $f_{1}(t) = f(t) + f(t - 2z_{0}/c) + f(t - 4z_{0}/c) + f(t - 6z_{0}/c) + \cdots$

$$= \sum_{k=0}^{\infty} f(t-2k\Xi_0/c)$$

 $f_2(t) = -\sum_{k=0}^{\infty} f(t-2(k+1)Z_0/c).$

All of these analytical results can be constructed very easily by graphical methods. (Figs. 2-3a)

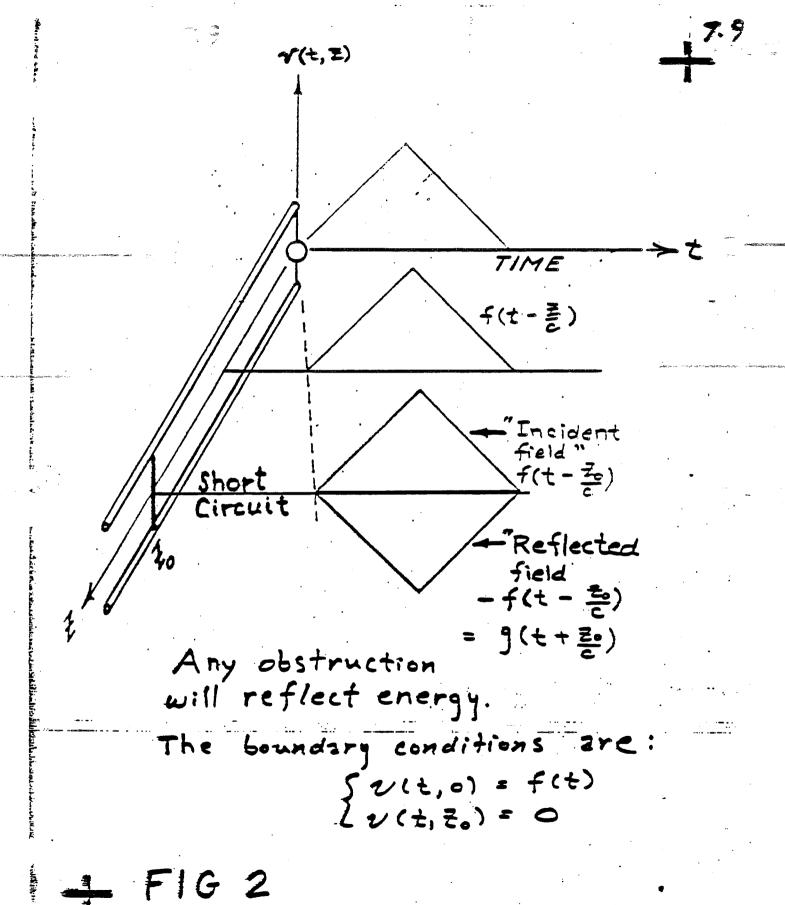

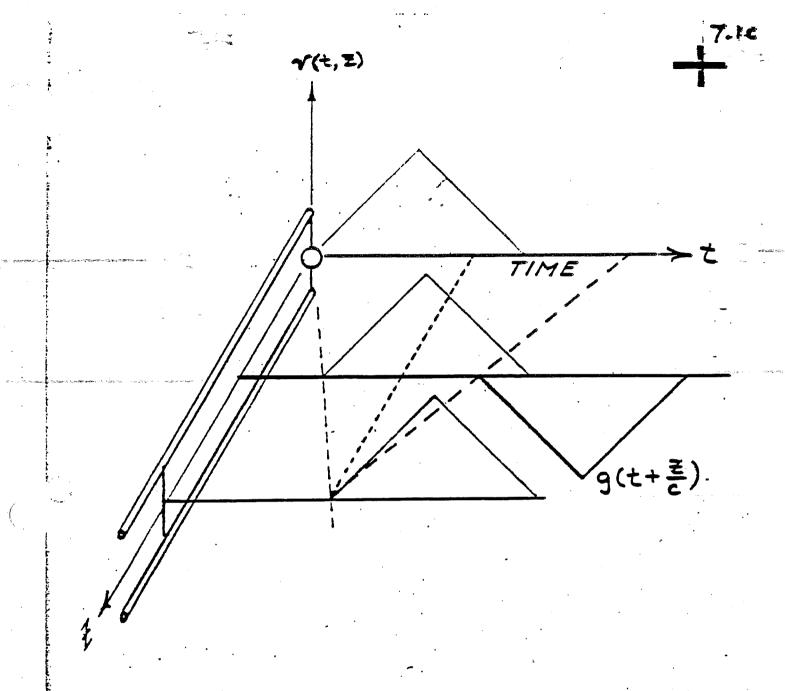


FIG. 3

TIME / (t+音) g(t+를).

+ FIG. 3a

The boundary conditions for a transmission line excited by a voltage source at z=0 of f(t) and loaded at z=z₀ with an open are:

$$v(t, 0) = f(t)$$

 $i(t, z_0) = 0$.

Again we must assume both positive and negative going waves. Applying the boundary condition on the current, we find that $f_1(t-z_0/c)=f_2(t+z_0/c)$ and hence the incident and reflected voltages add at the open.

Figure 4 shows the graphically constructed solution to this. problem.

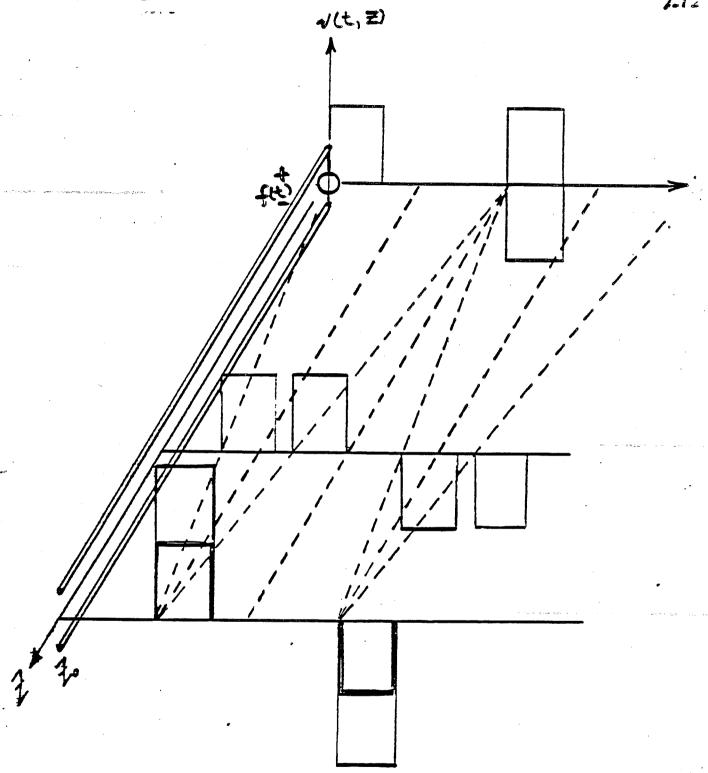


FIG 4

The boundary conditions in this case are:

$$v(t,0) = f(t)$$

 $v(t, z_0) = Ri(t, z_0),$



where R is the load resistance.

Applying the boundary condition at the load.

$$f_1(t-z_0/c) + f_2(t+z_0/c) = RY_0 f_1(t-z_0/c) - RY_0 f_2(t+z_0/c)$$

$$\frac{f_2(t+z_0/c)}{f_1(t-z_0/c)} = \frac{1-RY_0}{1+RY_0} = \Gamma.$$

The ratio of f_2 (t+z_o/c) to f_1 (t-z_o/c) is called the "reflection coefficient" since it is the fraction of the incident voltage that is reflected back toward the source.

Applying the boundary condition at the source, we obtain

$$f_i(t) + f_2(t) = f(t)$$

But
$$f_2(t+z_0/c) = \Gamma f_1(t-z_0/c) \Rightarrow$$

=
$$f(t) - \Gamma f(t - ZZ_0/c) + \Gamma^2 f(t - 4Z_0/c)$$

$$= \sum_{k=0}^{\infty} f(t - 2kZ_0/c) (-\Gamma)^k$$

Therefore,
$$v(t, \bar{z}) = f_1(t - \bar{z}/c) + f_2(t + \bar{z}/c)$$

= $f(t - \bar{z}/c) + \sum_{k=1}^{\infty} (-\Gamma)^k$

$$\left\{ f\left[t - \left(\frac{z + 2xz_0}{c}\right)\right] - f\left[t + \left(\frac{z - 2xz_0}{c}\right)\right] \right\}$$