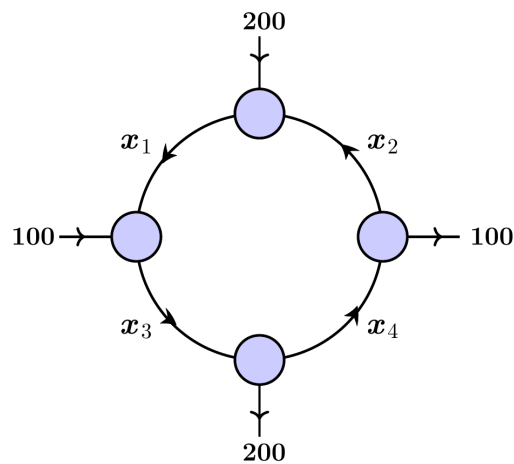


## Solution

### Section 1.8 – Applications

#### Exercise

The flow of traffic, in vehicles per hour, through a network of streets as is shown below



- a) Solve this system for  $x_i$ ,  $i = 1, 2, 3, 4$ .
- b) Find the traffic flow when  $x_4 = 0$ .
- c) Find the traffic flow when  $x_4 = 100$ .
- d) Find the traffic flow when  $x_1 = 2x_2$ .

#### Solution

$$a) \begin{cases} x_1 + 100 = x_3 \\ x_2 + 200 = x_1 \\ x_2 + 100 = x_4 \\ x_4 + 200 = x_3 \end{cases}$$

$$\begin{cases} -x_1 + x_3 = 100 \\ x_1 - x_2 = 200 \\ -x_2 + x_4 = 100 \\ x_3 - x_4 = 200 \end{cases}$$

$$\left( \begin{array}{cccc|c} -1 & 0 & 1 & 0 & 100 \\ 1 & -1 & 0 & 0 & 200 \\ 0 & -1 & 0 & 1 & 100 \\ 0 & 0 & 1 & -1 & 200 \end{array} \right) \quad R_2 + R_1$$

$$\left( \begin{array}{cccc|c} -1 & 0 & 1 & 0 & 100 \\ 0 & -1 & 1 & 0 & 300 \\ 0 & -1 & 0 & 1 & 100 \\ 0 & 0 & 1 & -1 & 200 \end{array} \right) \quad R_3 - R_2$$

$$\left( \begin{array}{cccc|c} -1 & 0 & 1 & 0 & 100 \\ 0 & -1 & 1 & 0 & 300 \\ 0 & 0 & -1 & 1 & -200 \\ 0 & 0 & 1 & -1 & 200 \end{array} \right) \quad R_4 + R_3$$

$$\left( \begin{array}{cccc|c} -1 & 0 & 1 & 0 & 100 \\ 0 & -1 & 1 & 0 & 300 \\ 0 & 0 & -1 & 1 & -200 \\ 0 & 0 & 0 & 0 & 0 \end{array} \right)$$

Let  $x_4$  be the free variable

$$\left\{ \begin{array}{l} \underline{x_3 = x_4 + 200} \\ \underline{x_2 = x_4 - 100} \\ x_1 = 200 + x_2 = \underline{x_4 + 100} \end{array} \right.$$

**Solution:**  $(x_4 + 100, x_4 - 100, x_4 + 200, x_4)$

**b)** The traffic flow when  $x_4 = 0$  is:

$$\therefore (100, -100, 200, 0)$$

**c)** The traffic flow when  $x_4 = 100$  is:

$$\therefore (200, 0, 300, 100)$$

**d)** The traffic flow when  $x_1 = 2x_2$  :

$$x_4 + 100 = 2(x_4 - 100)$$

$$x_4 + 100 = 2x_4 - 200$$

$$x_4 = 300$$

$$\therefore (400, 200, 500, 300)$$


## Exercise

Through a network, Express  $x_n$  's in terms of the parameters  $s$  and  $t$ .
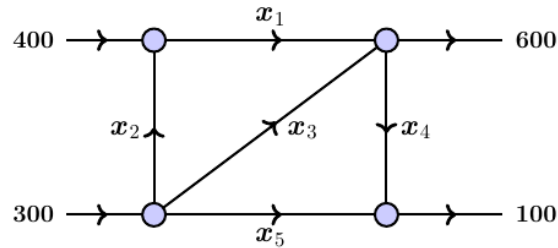
## Solution

$$\begin{cases} x_1 = x_2 + 400 \\ x_1 + x_3 = x_4 + 600 \\ x_4 + x_5 = 100 \\ x_2 + x_3 + x_5 = 300 \end{cases}$$

$$\begin{cases} x_1 - x_2 = 400 \\ x_2 + x_3 - x_4 = 600 \\ x_4 + x_5 = 100 \\ x_2 + x_3 + x_5 = 300 \end{cases}$$



$$\left( \begin{array}{ccccc|c} 1 & -1 & 0 & 0 & 0 & 400 \\ 1 & 0 & 1 & -1 & 0 & 600 \\ 0 & 0 & 0 & 1 & 1 & 100 \\ 0 & 1 & 1 & 0 & 1 & 300 \end{array} \right) \quad \begin{array}{l} R_2 - R_1 \\ R_3 \leftrightarrow R_4 \end{array}$$

$$\left( \begin{array}{ccccc|c} 1 & -1 & 0 & 0 & 0 & 400 \\ 0 & 1 & 1 & -1 & 0 & 200 \\ 0 & 1 & 1 & 0 & 1 & 300 \\ 0 & 0 & 0 & 1 & 1 & 100 \end{array} \right) \quad R_3 - R_2$$

$$\left( \begin{array}{ccccc|c} 1 & -1 & 0 & 0 & 0 & 400 \\ 0 & 1 & 1 & -1 & 0 & 200 \\ 0 & 0 & 0 & 1 & 1 & 100 \\ 0 & 0 & 0 & 1 & 1 & 100 \end{array} \right) \quad R_4 - R_3$$

$$\left( \begin{array}{ccccc|c} 1 & -1 & 0 & 0 & 0 & 400 \\ 0 & 1 & 1 & -1 & 0 & 200 \\ 0 & 0 & 0 & 1 & 1 & 100 \\ 0 & 0 & 0 & 0 & 0 & 0 \end{array} \right) \quad \begin{array}{l} x_1 - x_2 = 400 \quad \rightarrow x_1 = 400 + x_2 \\ x_2 + x_3 - x_4 = 200 \quad \rightarrow x_2 = 200 - x_3 + x_4 \\ x_4 + x_5 = 100 \quad \rightarrow \underline{x_4 = 100 - t} \end{array}$$


Let  $x_5 = t$  &  $x_3 = s$

$$x_2 = 200 - s + 100 - t = \underline{300 - s - t}$$

$$x_1 = 400 + 300 - s - t = \underline{700 - s - t}$$
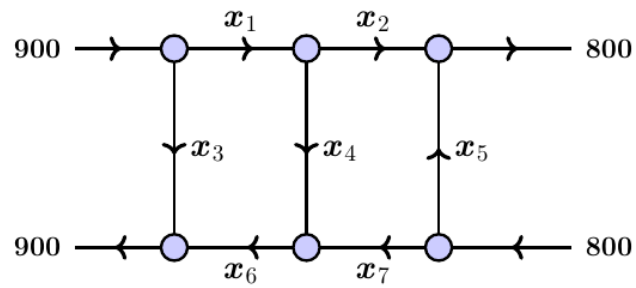
### Exercise

Water is flowing through a network of pipes. Express  $x_n$ 's in terms of the parameters  $s$  and  $t$ .



### Solution

$$x_1 + x_3 = 900$$

$$x_1 = x_2 + x_4 \rightarrow x_1 - x_2 - x_4 = 0$$

$$x_2 + x_5 = 800$$

$$x_5 + x_7 = 800$$

$$x_6 = x_4 + x_7 \rightarrow x_4 - x_6 + x_7 = 0$$

$$x_3 + x_6 = 900$$

$$\left[ \begin{array}{ccccccc|c} 1 & 0 & 1 & 0 & 0 & 0 & 0 & 900 \\ 1 & -1 & 0 & -1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 1 & 0 & 0 & 800 \\ 0 & 0 & 0 & 0 & 1 & 0 & 1 & 800 \\ 0 & 0 & 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 1 & 0 & 0 & 1 & 0 & 900 \end{array} \right] \quad R_2 - R_1$$

$$\left[ \begin{array}{ccccccc|c} 1 & 0 & 1 & 0 & 0 & 0 & 0 & 900 \\ 0 & -1 & -1 & -1 & 0 & 0 & 0 & -900 \\ 0 & 1 & 0 & 0 & 1 & 0 & 0 & 800 \\ 0 & 0 & 0 & 0 & 1 & 0 & 1 & 800 \\ 0 & 0 & 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 1 & 0 & 0 & 1 & 0 & 900 \end{array} \right] \quad \begin{array}{l} R_3 + R_2 \\ R_6 \\ R_4 \end{array}$$

$$\left[ \begin{array}{ccccccc|c} 1 & 0 & 1 & 0 & 0 & 0 & 0 & 900 \\ 0 & -1 & -1 & -1 & 0 & 0 & 0 & -900 \\ 0 & 0 & -1 & -1 & 1 & 0 & 0 & -100 \\ 0 & 0 & 1 & 0 & 0 & 1 & 0 & 900 \\ 0 & 0 & 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 1 & 800 \end{array} \right] \quad \begin{array}{l} -R_2 \\ R_4 + R_3 \end{array}$$

$$\left[ \begin{array}{ccccccc|c} 1 & 0 & 1 & 0 & 0 & 0 & 0 & 900 \\ 0 & 1 & 1 & 1 & 0 & 0 & 0 & 900 \\ 0 & 0 & -1 & -1 & 1 & 0 & 0 & -100 \\ 0 & 0 & 0 & -1 & 1 & 1 & 0 & 800 \\ 0 & 0 & 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 1 & 800 \end{array} \right] \quad R_5 + R_4$$

$$\left[ \begin{array}{ccccccc|c} 1 & 0 & 1 & 0 & 0 & 0 & 0 & 900 \\ 0 & 1 & 1 & 1 & 0 & 0 & 0 & 900 \\ 0 & 0 & -1 & -1 & 1 & 0 & 0 & -100 \\ 0 & 0 & 0 & -1 & 1 & 1 & 0 & 800 \\ 0 & 0 & 0 & 0 & 1 & 0 & 1 & 800 \\ 0 & 0 & 0 & 0 & 1 & 0 & 1 & 800 \end{array} \right] \quad R_6 - R_5$$

$$\left[ \begin{array}{ccccccc|c} 1 & 0 & 1 & 0 & 0 & 0 & 0 & 900 \\ 0 & 1 & 1 & 1 & 0 & 0 & 0 & 900 \\ 0 & 0 & -1 & -1 & 1 & 0 & 0 & -100 \\ 0 & 0 & 0 & -1 & 1 & 1 & 0 & 800 \\ 0 & 0 & 0 & 0 & 1 & 0 & 1 & 800 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{array} \right] \quad \begin{array}{l} x_2 = 900 - x_3 \quad (5) \\ x_2 = 900 - x_3 - x_4 \quad (4) \\ x_3 = 100 - x_4 + x_5 \quad (3) \\ -x_4 = 800 - x_5 - x_6 \quad (2) \\ x_5 = 800 - x_7 \quad (1) \end{array}$$

Let  $x_6 = s$  &  $x_7 = t$

(1)  $\rightarrow x_5 = 800 - t$

(2)  $\rightarrow x_4 = s - t$

(3)  $\rightarrow x_3 = 900 - s$


(2)  $\rightarrow x_2 = t$

(1)  $\rightarrow x_1 = s$

**Solution:**  $(s, t, 900-s, s-t, 800-t, s, t)$
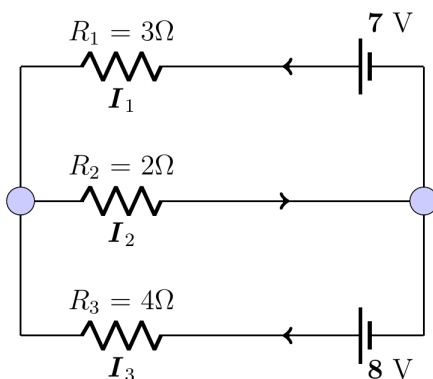
### Exercise

Determine the currents  $I_1$ ,  $I_2$ , and  $I_3$  for the electrical network shown below



### Solution

$$I_2 = I_1 + I_3$$

$$3I_1 + 2I_2 = 7$$

$$2I_2 + 4I_3 = 8$$

$$\begin{cases} I_1 - I_2 + I_3 = 0 \\ 3I_1 + 2I_2 = 7 \\ I_2 + 2I_3 = 4 \end{cases}$$

$$D = \begin{vmatrix} 1 & -1 & 1 \\ 3 & 2 & 0 \\ 0 & 1 & 2 \end{vmatrix} = 13 \quad D_1 = \begin{vmatrix} 0 & -1 & 1 \\ 7 & 2 & 0 \\ 4 & 1 & 2 \end{vmatrix} = 13 \quad D_2 = \begin{vmatrix} 1 & 0 & 1 \\ 3 & 7 & 0 \\ 0 & 4 & 2 \end{vmatrix} = 26 \quad D_3 = \begin{vmatrix} 1 & -1 & 0 \\ 3 & 2 & 7 \\ 0 & 1 & 4 \end{vmatrix} = 13$$

$$\underline{I_1 = 1 \text{ A}} \quad \underline{I_2 = 2 \text{ A}} \quad \underline{I_3 = 1 \text{ A}}$$

OR

$$\left( \begin{array}{ccc|c} 1 & -1 & 1 & 0 \\ 3 & 2 & 0 & 7 \\ 0 & 1 & 2 & 4 \end{array} \right) \quad R_2 - 3R_1$$


$$\left( \begin{array}{ccc|c} 1 & -1 & 1 & 0 \\ 0 & 5 & -3 & 7 \\ 0 & 1 & 2 & 4 \end{array} \right) \quad -5R_3 + R_2$$

$$\left( \begin{array}{ccc|c} 1 & -1 & 1 & 0 \\ 0 & 5 & -3 & 7 \\ 0 & 0 & -13 & -13 \end{array} \right) \quad \begin{array}{l} I_1 = I_2 - I_3 \\ 5I_2 = 3I_3 + 7 \\ \underline{I_3 = 1} \end{array}$$

$$\underline{I_2 = 2} \quad \underline{I_1 = 1}$$
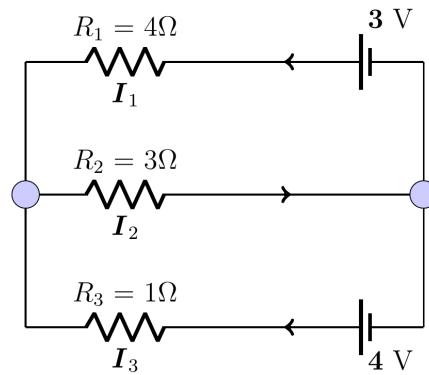
### Exercise

Determine the currents  $I_1$ ,  $I_2$ , and  $I_3$  for the electrical network shown below



### Solution

$$I_2 = I_1 + I_3$$

$$4I_1 + 3I_2 = 3$$

$$3I_2 + I_3 = 4$$

$$\begin{cases} I_1 - I_2 + I_3 = 0 \\ 4I_1 + 3I_2 = 3 \\ 3I_2 + I_3 = 4 \end{cases}$$

$$D = \begin{vmatrix} 1 & -1 & 1 \\ 4 & 3 & 0 \\ 0 & 3 & 1 \end{vmatrix} = 19$$

$$D_1 = \begin{vmatrix} 0 & -1 & 1 \\ 3 & 3 & 0 \\ 4 & 3 & 1 \end{vmatrix} = 0$$

$$D_2 = \begin{vmatrix} 1 & 0 & 1 \\ 4 & 3 & 0 \\ 0 & 4 & 1 \end{vmatrix} = 19$$

$$D_3 = \begin{vmatrix} 1 & -1 & 0 \\ 4 & 3 & 3 \\ 0 & 3 & 4 \end{vmatrix} = 19$$

$$\underline{I_1 = 0 \text{ A}} \quad \underline{I_2 = 1 \text{ A}} \quad \underline{I_3 = 1 \text{ A}}$$

**OR**

$$\left( \begin{array}{ccc|c} 1 & -1 & 1 & 0 \\ 4 & 3 & 0 & 3 \\ 0 & 3 & 1 & 4 \end{array} \right) \quad R_2 - 4R_1$$

$$\left( \begin{array}{ccc|c} 1 & -1 & 1 & 0 \\ 0 & 7 & -4 & 3 \\ 0 & 3 & 1 & 4 \end{array} \right) \quad 7R_3 - 3R_2$$


$$\left( \begin{array}{ccc|c} 1 & -1 & 1 & 0 \\ 0 & 7 & -4 & 3 \\ 0 & 0 & 19 & 19 \end{array} \right) \quad \begin{array}{l} \rightarrow I_1 = I_2 - I_3 \quad (2) \\ \rightarrow 7I_2 = 4I_3 + 3 \quad (1) \end{array}$$

$$\underline{I_3 = 1}$$

$$\underline{I_2 = 1} \quad \underline{I_1 = 0}$$
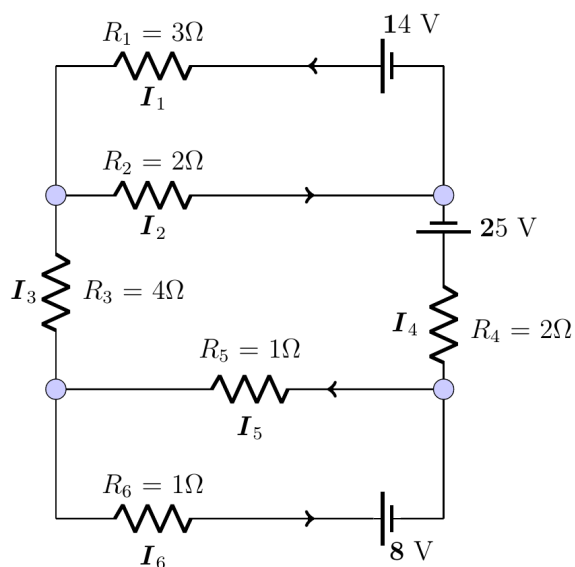
## Exercise

Determine the currents  $I_1$ ,  $I_2$ ,  $I_3$ ,  $I_4$ ,  $I_5$ , and  $I_6$  for the electrical network shown below



## Solution

$$I_1 + I_3 = I_2 \rightarrow I_1 - I_2 + I_3 = 0$$

$$I_1 + I_4 = I_2 \rightarrow I_1 - I_2 + I_4 = 0$$

$$I_3 + I_6 = I_5 \rightarrow I_3 - I_5 + I_6 = 0$$

$$\begin{cases} 3I_1 + 2I_2 = 14 \\ 2I_2 + 4I_3 + I_5 + 2I_4 = 25 \\ I_5 + I_6 = 8 \end{cases}$$

$$\left[ \begin{array}{cccccc|c} 1 & -1 & 1 & 0 & 0 & 0 & 0 \\ 1 & -1 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & -1 & 1 & 0 \\ 3 & 2 & 0 & 0 & 0 & 0 & 14 \\ 0 & 2 & 4 & 2 & 1 & 0 & 25 \\ 0 & 0 & 0 & 0 & 1 & 1 & 8 \end{array} \right] \quad \begin{array}{l} R_2 - R_1 \\ R_4 - 3R_1 \end{array}$$

$$\left[ \begin{array}{cccccc|c} 1 & -1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 5 & -3 & 0 & 0 & 0 & 14 \\ 0 & 2 & 4 & 2 & 1 & 0 & 25 \\ 0 & 0 & 0 & 0 & 1 & 1 & 8 \end{array} \right] \quad \begin{array}{l} R_4 \\ R_2 \\ R_3 \end{array}$$



$$\left[ \begin{array}{cccccc|c} 1 & -1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 5 & -3 & 0 & 0 & 0 & 14 \\ 0 & 2 & 4 & 2 & 1 & 0 & 25 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 & 1 & 8 \end{array} \right] \quad \begin{array}{l} 5R_3 - 2R_2 \\ \\ R_5 + R_4 \end{array}$$

$$\left[ \begin{array}{cccccc|c} 1 & -1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 5 & -3 & 0 & 0 & 0 & 14 \\ 0 & 0 & 26 & 10 & 5 & 0 & 97 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & -1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 & 1 & 8 \end{array} \right] \quad 26R_4 + R_3$$


$$\left[ \begin{array}{cccccc|c} 1 & -1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 5 & -3 & 0 & 0 & 0 & 14 \\ 0 & 0 & 26 & 10 & 5 & 0 & 97 \\ 0 & 0 & 0 & 36 & 5 & 0 & 97 \\ 0 & 0 & 0 & 1 & -1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 & 1 & 8 \end{array} \right] \quad 36R_5 - R_4$$

$$\left[ \begin{array}{cccccc|c} 1 & -1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 5 & -3 & 0 & 0 & 0 & 14 \\ 0 & 0 & 26 & 10 & 5 & 0 & 97 \\ 0 & 0 & 0 & 36 & 5 & 0 & 97 \\ 0 & 0 & 0 & 0 & -41 & 36 & -97 \\ 0 & 0 & 0 & 0 & 1 & 1 & 8 \end{array} \right] \quad 41R_6 + R_5$$

$$\left[ \begin{array}{cccccc|c} 1 & -1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 5 & -3 & 0 & 0 & 0 & 14 \\ 0 & 0 & 26 & 10 & 5 & 0 & 97 \\ 0 & 0 & 0 & 36 & 5 & 0 & 97 \\ 0 & 0 & 0 & 0 & -41 & 36 & -97 \\ 0 & 0 & 0 & 0 & 0 & 77 & 231 \end{array} \right] \quad \begin{array}{ll} I_1 = 4 - 2 & \rightarrow \underline{I_1 = 2} \\ 5I_2 = 14 + 3(2) & \rightarrow \underline{I_2 = 4} \\ 26I_3 = 97 - 10(2) - 5(5) & \rightarrow \underline{I_3 = 2} \\ 36I_4 = 97 - 5(5) & \rightarrow \underline{I_4 = 2} \\ -41I_5 = -97 - 36(3) & \rightarrow \underline{I_5 = 5} \\ 77I_6 = 231 & \rightarrow \underline{I_6 = 3} \end{array}$$
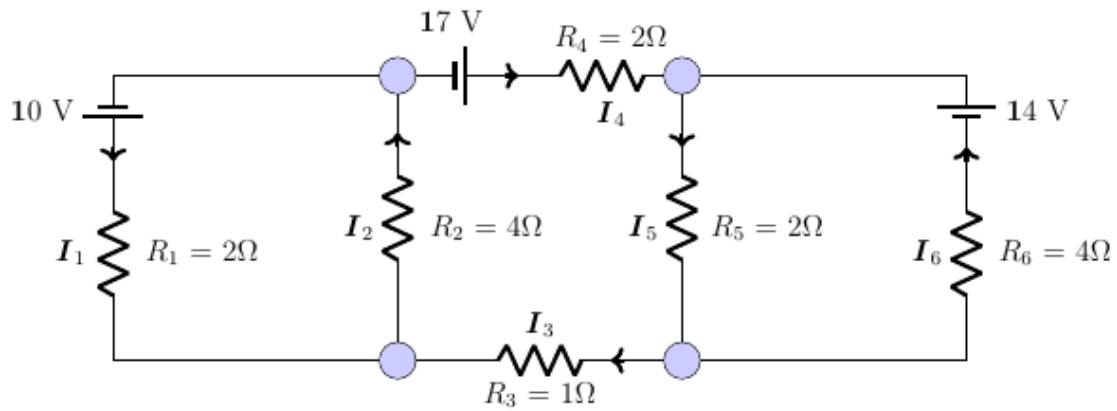
### Exercise

Determine the currents  $I_1$ ,  $I_2$ ,  $I_3$ ,  $I_4$ ,  $I_5$ , and  $I_6$  for the electrical network shown below



### Solution

$$1 \rightarrow I_1 + I_3 = I_2$$

$$2 \rightarrow I_1 + I_4 = I_2$$

$$3 \rightarrow I_3 + I_6 = I_5$$

$$4 \rightarrow I_4 + I_6 = I_5$$

$$\left\{ \begin{array}{l} I_1 - I_2 + I_3 = 0 \\ I_1 - I_2 + I_4 = 0 \\ I_3 - I_5 + I_6 = 0 \\ I_4 - I_5 + I_6 = 0 \\ 2I_1 + 4I_2 = 10 \\ 4I_2 + I_3 + 2I_4 + 2I_5 = 17 \\ 2I_5 + 4I_6 = 14 \end{array} \right.$$

$$\left( \begin{array}{cccccc|c} 1 & -1 & 1 & 0 & 0 & 0 & 0 \\ 1 & -1 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 0 & 1 & -1 & 1 & 0 \\ 1 & 2 & 0 & 0 & 0 & 0 & 5 \\ 0 & 4 & 1 & 2 & 2 & 0 & 17 \\ 0 & 0 & 0 & 0 & 1 & 2 & 7 \end{array} \right) \begin{array}{l} \\ R_2 - R_1 \\ \\ R_5 - R_1 \\ \end{array}$$

$$\begin{pmatrix} 1 & -1 & 1 & 0 & 0 & 0 & | & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & | & 0 \\ 0 & 0 & 1 & 0 & -1 & 1 & | & 0 \\ 0 & 0 & 0 & 1 & -1 & 1 & | & 0 \\ 0 & 3 & -1 & 0 & 0 & 0 & | & 5 \\ 0 & 4 & 1 & 2 & 2 & 0 & | & 17 \\ 0 & 0 & 0 & 0 & 1 & 2 & | & 7 \end{pmatrix} \quad \begin{array}{l} R_3 + R_2 \\ \\ \\ 3R_6 - 4R_5 \end{array}$$

$$\begin{pmatrix} 1 & -1 & 1 & 0 & 0 & 0 & | & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & | & 0 \\ 0 & 0 & 0 & 1 & -1 & 1 & | & 0 \\ 0 & 0 & 0 & 1 & -1 & 1 & | & 0 \\ 0 & 3 & -1 & 0 & 0 & 0 & | & 5 \\ 0 & 0 & 7 & 6 & 6 & 0 & | & 31 \\ 0 & 0 & 0 & 0 & 1 & 2 & | & 7 \end{pmatrix} \quad R_4 - R_3$$

$$\begin{pmatrix} 1 & -1 & 1 & 0 & 0 & 0 & | & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & | & 0 \\ 0 & 0 & 0 & 1 & -1 & 1 & | & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & | & 0 \\ 0 & 3 & -1 & 0 & 0 & 0 & | & 5 \\ 0 & 0 & 7 & 6 & 6 & 0 & | & 31 \\ 0 & 0 & 0 & 0 & 1 & 2 & | & 7 \end{pmatrix} \quad R_6 + 7R_2$$

$$\begin{pmatrix} 1 & -1 & 1 & 0 & 0 & 0 & | & 0 \\ 0 & 3 & -1 & 0 & 0 & 0 & | & 5 \\ 0 & 0 & -1 & 1 & 0 & 0 & | & 0 \\ 0 & 0 & 0 & 1 & -1 & 1 & | & 0 \\ 0 & 0 & 0 & 13 & 6 & 0 & | & 31 \\ 0 & 0 & 0 & 0 & 1 & 2 & | & 7 \\ 0 & 0 & 0 & 0 & 0 & 0 & | & 0 \end{pmatrix} \quad R_5 - 13R_4$$

$$\begin{pmatrix} 1 & -1 & 1 & 0 & 0 & 0 & | & 0 \\ 0 & 3 & -1 & 0 & 0 & 0 & | & 5 \\ 0 & 0 & -1 & 1 & 0 & 0 & | & 0 \\ 0 & 0 & 0 & 1 & -1 & 1 & | & 0 \\ 0 & 0 & 0 & 0 & 19 & -13 & | & 31 \\ 0 & 0 & 0 & 0 & 1 & 2 & | & 7 \\ 0 & 0 & 0 & 0 & 0 & 0 & | & 0 \end{pmatrix} \quad 19R_6 - R_5$$

$$\left( \begin{array}{cccccc|c} 1 & -1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 3 & -1 & 0 & 0 & 0 & 5 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & -1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 19 & -13 & 31 \\ 0 & 0 & 0 & 0 & 0 & 51 & 102 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{array} \right) \begin{array}{l} (4) \\ (3) \\ (2) \\ (1) \\ I_5 = \frac{1}{19}(31 + 13I_6) \\ \underline{I_6 = 2} \end{array}$$

$$\underline{I_5 = 3}$$

$$(1) \rightarrow \underline{I_4 = I_5 - I_6 = 1}$$

$$(2) \rightarrow \underline{I_3 = I_4 = 1}$$

$$(3) \rightarrow \underline{I_2 = \frac{1}{3}(I_3 + 5) = 2}$$

$$(4) \rightarrow \underline{I_1 = I_2 - I_3 = 1}$$

### Exercise

Consider the invertible matrix:  $A = \begin{pmatrix} 1 & 2 & 2 \\ 3 & 7 & 9 \\ -3 & -2 & 7 \end{pmatrix}$

The message: **ICEBERG DEAD AHEAD**

- Write the uncoded row matrices  $1 \times 3$  for the message.
- Use the matrix  $A$  to encode the message.
- Decode a message from part  $b$ ) given the matrix  $A$ .

### Solution

$$\begin{array}{l} a) \\ \begin{array}{c|c|c|c|c|c|c} 0 = \_ & 4 = D & 8 = H & 12 = L & 16 = P & 20 = T & 24 = X \\ 1 = A & 5 = E & 9 = I & 13 = M & 17 = Q & 21 = U & 25 = Y \\ 2 = B & 6 = F & 10 = J & 14 = N & 18 = R & 22 = V & 26 = Z \\ 3 = C & 7 = G & 11 = K & 15 = O & 19 = S & 23 = W & \end{array} \end{array}$$

$$\begin{array}{cccccc} I & C & E & B & E & R & G & \_ & D & E & A & D & \_ & A & H & E & A & D \\ [9 & 3 & 5] & [2 & 5 & 18] & [7 & 0 & 4] & [5 & 1 & 4] & [0 & 1 & 8] & [5 & 1 & 4] \end{array}$$

- Let encode the message **ICEBERG DEAD AHEAD**

$$\begin{bmatrix} 9 & 3 & 5 \end{bmatrix} \begin{bmatrix} 1 & 2 & 2 \\ 3 & 7 & 9 \\ -3 & -2 & 7 \end{bmatrix} = \begin{bmatrix} 3 & 29 & 80 \end{bmatrix}$$

$$\begin{bmatrix} 2 & 5 & 18 \end{bmatrix} \begin{bmatrix} 1 & 2 & 2 \\ 3 & 7 & 9 \\ -3 & -2 & 7 \end{bmatrix} = \begin{bmatrix} -37 & 3 & 175 \end{bmatrix}$$

$$\begin{bmatrix} 7 & 0 & 4 \end{bmatrix} \begin{bmatrix} 1 & 2 & 2 \\ 3 & 7 & 9 \\ -3 & -2 & 7 \end{bmatrix} = \begin{bmatrix} -5 & 6 & 42 \end{bmatrix}$$

$$\begin{bmatrix} 5 & 1 & 4 \end{bmatrix} \begin{bmatrix} 1 & 2 & 2 \\ 3 & 7 & 9 \\ -3 & -2 & 7 \end{bmatrix} = \begin{bmatrix} -4 & 9 & 47 \end{bmatrix}$$

$$\begin{bmatrix} 0 & 1 & 8 \end{bmatrix} \begin{bmatrix} 1 & 2 & 2 \\ 3 & 7 & 9 \\ -3 & -2 & 7 \end{bmatrix} = \begin{bmatrix} -21 & -5 & 65 \end{bmatrix}$$

$$\begin{bmatrix} 5 & 1 & 4 \end{bmatrix} \begin{bmatrix} 1 & 2 & 2 \\ 3 & 7 & 9 \\ -3 & -2 & 7 \end{bmatrix} = \begin{bmatrix} -4 & 9 & 47 \end{bmatrix}$$

The sequence of coded row matrices is

$$\begin{bmatrix} 3 & 29 & 80 \end{bmatrix} \begin{bmatrix} -37 & 3 & 175 \end{bmatrix} \begin{bmatrix} -5 & 6 & 42 \end{bmatrix} \begin{bmatrix} -4 & 9 & 47 \end{bmatrix} \begin{bmatrix} -21 & -5 & 65 \end{bmatrix} \begin{bmatrix} -4 & 9 & 47 \end{bmatrix}$$

The cryptogram:

$$3 \ 29 \ 80 \ -37 \ 3 \ 175 \ -5 \ 6 \ 42 \ -4 \ 9 \ 47 \ -21 \ -5 \ 65 \ -4 \ 9 \ 47$$

c) To decode a message given the matrix  $A$ .

$$|A| = \begin{vmatrix} 1 & 2 & 2 \\ 3 & 7 & 9 \\ -3 & -2 & 7 \end{vmatrix} = 1$$

$$A^{-1} = \begin{bmatrix} 67 & -18 & 4 \\ -48 & 13 & -3 \\ 15 & -4 & 1 \end{bmatrix}$$

With the cryptogram:

$$\begin{bmatrix} 3 & 29 & 80 \end{bmatrix} \begin{bmatrix} -37 & 3 & 175 \end{bmatrix} \begin{bmatrix} -5 & 6 & 42 \end{bmatrix} \begin{bmatrix} -4 & 9 & 47 \end{bmatrix} \begin{bmatrix} -21 & -5 & 65 \end{bmatrix} \begin{bmatrix} -4 & 9 & 47 \end{bmatrix}$$

$$\begin{bmatrix} 3 & 29 & 80 \end{bmatrix} \begin{bmatrix} 67 & -18 & 4 \\ -48 & 13 & -3 \\ 15 & -4 & 1 \end{bmatrix} = \begin{bmatrix} 9 & 3 & 5 \end{bmatrix}$$

$$\begin{bmatrix} -37 & 3 & 175 \end{bmatrix} \begin{bmatrix} 67 & -18 & 4 \\ -48 & 13 & -3 \\ 15 & -4 & 1 \end{bmatrix} = \begin{bmatrix} 2 & 5 & 18 \end{bmatrix}$$

$$\begin{bmatrix} -5 & 6 & 42 \end{bmatrix} \begin{bmatrix} 67 & -18 & 4 \\ -48 & 13 & -3 \\ 15 & -4 & 1 \end{bmatrix} = \begin{bmatrix} 7 & 0 & 1 \end{bmatrix}$$

$$\begin{bmatrix} -4 & 9 & 47 \end{bmatrix} \begin{bmatrix} 67 & -18 & 4 \\ -48 & 13 & -3 \\ 15 & -4 & 1 \end{bmatrix} = \begin{bmatrix} 5 & 1 & 4 \end{bmatrix}$$

$$\begin{bmatrix} -21 & -9 & 65 \end{bmatrix} \begin{bmatrix} 67 & -18 & 4 \\ -48 & 13 & -3 \\ 15 & -4 & 1 \end{bmatrix} = \begin{bmatrix} 0 & 1 & 8 \end{bmatrix}$$

$$\begin{bmatrix} -4 & 9 & 47 \end{bmatrix} \begin{bmatrix} 67 & -18 & 4 \\ -48 & 13 & -3 \\ 15 & -4 & 1 \end{bmatrix} = \begin{bmatrix} 5 & 1 & 4 \end{bmatrix}$$

The message is:

9 3 5 2 5 18 7 0 1 5 1 4 0 1 8 5 1 4  
*I C E B E R G \_ D E A D \_ A H E A D*